

Ch. 1: D.C. Circuits:

1. Differentiate between active & passive elements.

OR

State the 2 types of active elem. (Const. 'V' & Const. 'I')

&

state the 3 types of passive elem. (R, L & C)

2. State the 3 types of D.C. sources.

3. State the 2 types of A.C. sources.

4. Define R, L, C, X_L & X_C along with their units.

5. State the Ohm's Law for D.C. circuits.

6. State the " " " A.C. " "

7. State KCL & KVL for D.C. circuits.

8. State the difference between Mesh & Nodal Analysis.

9. What are limitations/disadvantages of Mesh Analysis?

10. What do you mean by linear elements? State their 3 types.

11. State & explain the Superposition, Thevenin's, M.P.T.T. & Norton's Theorems.

12. What is the application of M.P.T.T? (Public Address System)

Why is it not used for electrical machines like transformer?

13. Give/Write the proof of MPTT.

14. State the 2 types of electrical faults. (O.C. & S.C.)

15. Why X_L & X_C are not considered in D.C. circuits?

—X—

Ch. 2: A.C. Circuits:

1. Prove that pure L & C do not consume any power.

2. Define Av & RMS values, Form & Peak Factors

State their expressions/values for an alternating current.

3. Define cycle, frequency & time period.

4. For an A.C., prove that RMS Value > A.V. Value.

5. " " " " " Peak Factor > Form Factor

6. Draw labelled V- Δ , Z- Δ & P- Δ for R-L, R-C, R-L-C (with X_L & X_C)

8. Draw a neat labelled $P-\Delta$ for R-L/R-C circuit.

Mark on its sides the names, expressions & practical units of the respective powers.

9. Define Y , G & B alongwith their mathematical expressions

10. Sketch the graphs of R v/s f , X_L v/s f , X_C v/s f , Z v/s f & I v/s

11. Compare between Series & Parallel resonance.

12. Define dynamic impedance parallel resonance circuit

13. Define Q-factor & Bandwidth. State their expressions.

—X—

Ch. 3: Three Phase Circuits:

1. Advantages of 3- ϕ circuits.

2. Compare between 3- ϕ Y & Δ connections

3. Draw typical phasor dgm's for Y & Δ connections

4. State uses/applications of Y & Δ connections.

5. Draw a labelled total power Δ for 3- ϕ system.

6. Advantages of 2 watt-meter method

or

How can we measure power in 3- ϕ circuit with 2 wattmeters?

7. Why a single 3- ϕ system is more economical than three separate 1- ϕ systems? Explain in brief.

8. State the expressions for total power P_T , total reactive power Q_T , p.f. in terms of the 2 wattmeter readings W_1 & W_2 .

9. What precautions will you take if one of the two wattmeters say W_1 starts reading -ve?

10. How can you decide the nature of the 3- ϕ load from the readings W_1 & W_2 of the 2 wattmeters?

—X—

Ch.4:Transformer (Abbreviated as 'Xr')

1. State the principle of a 1- ϕ transformer.
2. State features of a 1- ϕ Xr.
3. Define ideal & practical Xr
4. State EMF equations.
5. Define turns ratio, voltage ratio & current ratio.
6. Draw phasor dgm's of ideal & practical Xrs on no load.

2

1



7. Draw phasor dgm's of a practical Xr supplying resistive, inductive & capacitive loads.

8. Define efficiency of a Xr

9. State the condition for max. efficiency & prove.

10. Define % Voltage regulation & state its practical values for inductive & capacitive loads.

11. State the purposes of O.C. & S.C. Tests of a Xr.

12. State & explain the 2 types of losses in a Xr.

13. Sketch/develop the equivalent ckt of a Xr w.r.t. py. & label the same.

14. How the eq. ckt helps in calculating the 4 parameters of the Xr viz. X_0, R_0, X_{01} & R_{01} ?

15. What will happen if we apply D.C. voltage on the py of a Xr instead of A.C. voltage ?

16. Why Xr rating is given in kVA & not in kW ?

—X—